

The circuit shown above left is made up of a variable resistor and a battery with negligible internal resistance. A graph of the power  $P$  dissipated in the resistor as a function of the current  $I$  ...